

# Instruction Sequencer FSM

By Sidhardh Burre

CS/ECE 2330 Digital Logic Design

March 20, 2021

# Table of Contents

## Contents

1 Problem Statement.....	1
2 Analytical Design.....	3
3 Numerical Verification .....	4
4 Summary.....	5

## Table of Figures

Figure 1: Simple CPU Instruction Format.....	Error! Bookmark not defined.
Figure 2: Truth Table and Logical Expressions for Opcode Decoder .....	Error! Bookmark not defined.
Figure 3: Circuit for Opcode Decoder .....	Error! Bookmark not defined.
Figure 4: Input Test Vectors .....	Error! Bookmark not defined.
Figure 5: Test Results (Table).....	Error! Bookmark not defined.
Figure 6: Test Results (Graph).....	Error! Bookmark not defined.


## 1 Problem Statement

Design a circuit to generate the instruction sequencing signals used to ensure the proper sequencing of the control signals generation for instruction fetch and execute, completing the control unit design.

The circuit in question is a Finite State Machine (FSM) with 3 inputs (the 3-bit opcode) and requires 3 sequential elements to store the current state. A state transition table for the circuit is shown in Table 1, each 'x' indicates a "don't care". Additionally, a state transition diagram is shown in Figure 1.


Inputs: Opcode Current State	Next State							
	Load (000)	Store (001)	Add (010)	Sub (011)	Inc (100)	Dec (101)	Bra (110)	Beq (111)
000	001	001	001	001	001	001	001	001
001	010	010	010	010	010	010	010	010
010	011	011	011	011	011	011	011	011
011	100	100	100	100	100	100	100	100
100	101	101	101	101	101	101	000	000
101	000	000	110	110	110	110	x	x
110	x	x	111	111	111	111	x	x
111	x	x	000	000	000	000	x	x

Table 1: Simple CPU Sequencer FSM State Transition Table

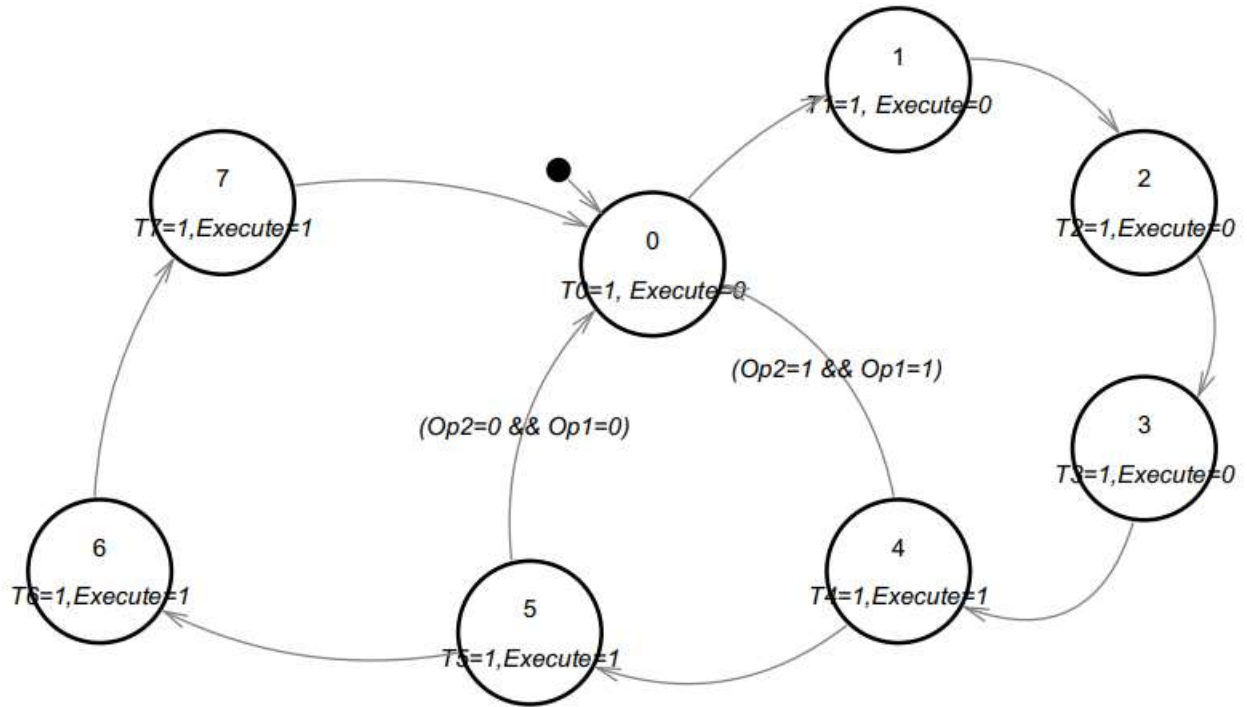

**Figure 1: State Transition Diagram**

The purpose of this circuit is to generate the 8 timing pulses that are used to sequence the instruction fetch and execute operations. A typical set of outputs is shown in Figure 2, for an instruction that requires 8 steps to complete. The output table for the timing pulses is shown in Table 2 for 8 instructions.

 

**Figure 2: Timing Pulses for One Instruction Cycle**

Inputs: Opcode Current State		Output: T0-T7							
		Load (000)	Store (001)	Add (010)	Sub (011)	Inc (100)	Dec (101)	Bra (110)	Beq (111)
000		T0	T0	T0	T0	T0	T0	T0	T0
001		T1	T1	T1	T1	T1	T1	T1	T1
010		T2	T2	T2	T2	T2	T2	T2	T2
011		T3	T3	T3	T3	T3	T3	T3	T3
100		T4	T4	T4	T4	T4	T4	T4	T4
101		T5	T5	T5	T5	T5	T5	x	x
110		x	x	T6	T6	T6	T6	x	x
111		x	x	T7	T7	T7	T7	x	x

**Table 2: Output Table for Timing Pulses**

Additionally, the circuit must generate a signal to indicate when an instruction is being fetched and when it is being executed. The output table for Execute is shown in Table 3.

Inputs: Opcode Current State		Output: Execute							
		Load (000)	Store (001)	Add (010)	Sub (011)	Inc (100)	Dec (101)	Bra (110)	Beq (111)
000		0	0	0	0	0	0	0	0
001		0	0	0	0	0	0	0	0
010		0	0	0	0	0	0	0	0
011		0	0	0	0	0	0	0	0
100		1	1	1	1	1	1	1	1
101		1	1	1	1	1	1	x	x
110		x	x	1	1	1	1	x	x
111		x	x	1	1	1	1	x	x

**Table 3: Output Table for Execute**


## 2 Analytical Design

The truth table for the Instruction Sequencer FSM is shown in Figure 3 along with the logical equations that allow the input to be converted into the corresponding signal.

File New Edit Create KMap														All possible solutions	
Q2n	Q1n	Q0n	Q2n+1	Q1n+1	Q0n+1	T0	T1	T2	T3	T4	T5	T6	T7	Exec	
0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	$Q_2^{n+1} = (Op1 \wedge \overline{Op2} \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op1} \wedge Op2 \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op1} \wedge \overline{Q_0^n} \wedge Q_0^n) \vee (\overline{Op2} \wedge \overline{Q_0^n} \wedge Q_0^n) \vee (Q_0^n \wedge Q_1^n \wedge \overline{Q_0^n})$
0	0	0	0	0	1	0	0	1	1	0	0	0	0	0	$Q_1^{n+1} = (Op1 \wedge \overline{Op2} \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op1} \wedge Op2 \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op1} \wedge \overline{Q_0^n} \wedge Q_0^n) \vee (Q_0^n \wedge Q_1^n \wedge \overline{Q_0^n}) \vee (Q_0^n \wedge Q_1^n \wedge Q_0^n)$
0	0	0	0	1	0	0	0	1	1	0	0	0	0	0	$Q_0^{n+1} = (Op1 \wedge \overline{Op2} \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op1} \wedge Op2 \wedge \overline{Q_1^n} \wedge Q_0^n) \vee (\overline{Op2} \wedge \overline{Q_0^n} \wedge Q_0^n) \vee (Q_0^n \wedge Q_1^n \wedge \overline{Q_0^n}) \vee (Q_0^n \wedge Q_1^n \wedge Q_0^n)$
0	0	0	0	1	1	0	0	1	1	0	0	0	0	0	$Q_1^n = (Op1 \wedge Q_0^n \wedge \overline{Q_1^n}) \vee (Op2 \wedge Q_0^n \wedge \overline{Q_1^n}) \vee (Q_0^n \wedge \overline{Q_1^n} \wedge \overline{Q_0^n}) \vee (Q_0^n \wedge Q_1^n)$
0	0	0	1	0	0	0	1	1	0	0	0	0	0	0	$Q_0^{n+1} = (\overline{Op1} \wedge \overline{Q_0^n}) \vee (\overline{Op2} \wedge \overline{Q_0^n}) \vee (\overline{Q_0^n} \wedge \overline{Q_0^n})$
0	0	0	1	0	1	0	0	1	0	0	0	0	0	0	$T0 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	0	0	0	0	1	0	0	0	0	0	0	0	$T1 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	0	0	1	0	0	1	0	0	0	0	0	0	$T2 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	0	1	0	0	1	0	0	0	0	0	0	0	$T3 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	0	1	1	0	0	1	0	0	0	0	0	0	$T4 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	$T5 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	1	0	1	0	0	1	0	0	0	0	0	0	$T6 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	0	1	1	1	0	0	1	0	0	0	0	0	0	0	$T7 = Q_0^n \wedge Q_1^n \wedge \overline{Q_2^n}$
0	1	0	0	0	0	0	1	1	0	0	0	0	0	0	$Execute = Q_0^n$
0	1	0	0	0	1	0	1	1	0	0	0	0	0	0	
0	1	0	0	1	0	0	1	0	0	0	0	0	0	0	
0	1	0	0	1	1	0	0	1	0	0	0	0	0	0	
0	1	0	1	0	0	0	1	0	0	0	0	0	0	0	
0	1	0	1	0	1	0	0	1	0	0	0	0	0	0	
0	1	0	1	1	0	0	1	0	0	0	0	0	0	0	
0	1	0	1	1	1	0	0	1	0	0	0	0	0	0	
0	1	1	0	0	0	0	1	1	0	0	0	0	0	0	
0	1	1	0	0	1	0	1	1	0	0	0	0	0	0	
0	1	1	0	1	0	0	1	0	0	0	0	0	0	0	
0	1	1	0	1	1	0	0	1	0	0	0	0	0	0	
0	1	1	1	0	0	0	1	0	0	0	0	0	0	0	
0	1	1	1	0	1	0	0	0	0	0	0	0	0	0	
0	1	1	1	1	0	0	0	0	0	0	0	0	0	0	
0	1	1	1	1	1	0	0	0	0	0	0	0	0	0	
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	
1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	
1	0	0	0	1	1	0	0	0	0	0	0	0	0	0	
1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	
1	0	0	1	0	1	0	0	0	0	0	0	0	0	0	
1	0	0	1	1	0	0	0	0	0	0	0	0	0	0	
1	0	0	1	1	1	0	0	0	0	0	0	0	0	0	
1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	
1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	
1	0	1	0	1	0	0	0	0	0	0	0	0	0	0	
1	0	1	0	1	1	0	0	0	0	0	0	0	0	0	
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	
1	0	1	1	0	1	0	0	0	0	0	0	0	0	0	
1	0	1	1	1	0	0	0	0	0	0	0	0	0	0	
1	0	1	1	1	1	0	0	0	0	0	0	0	0	0	
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	
1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	
1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	
1	1	0	0	1	1	0	0	0	0	0	0	0	0	0	
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	
1	1	0	1	0	1	0	0	0	0	0	0	0	0	0	
1	1	0	1	1	0	0	0	0	0	0	0	0	0	0	
1	1	0	1	1	1	0	0	0	0	0	0	0	0	0	
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	
1	1	1	0	1	0	0	0	0	0	0	0	0	0	0	
1	1	1	0	1	1	0	0	0	0	0	0	0	0	0	
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	
1	1	1	1	0	1	0	0	0	0	0	0	0	0	0	
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	
1	1	1	1	1	1	0	0	0	0	0	0	0	0	0	

**Figure 3: Truth Table and Logical Expressions for Instruction Sequencer FSM**

The logical expressions were analyzed to form the circuit schematic shown in Figure 4.

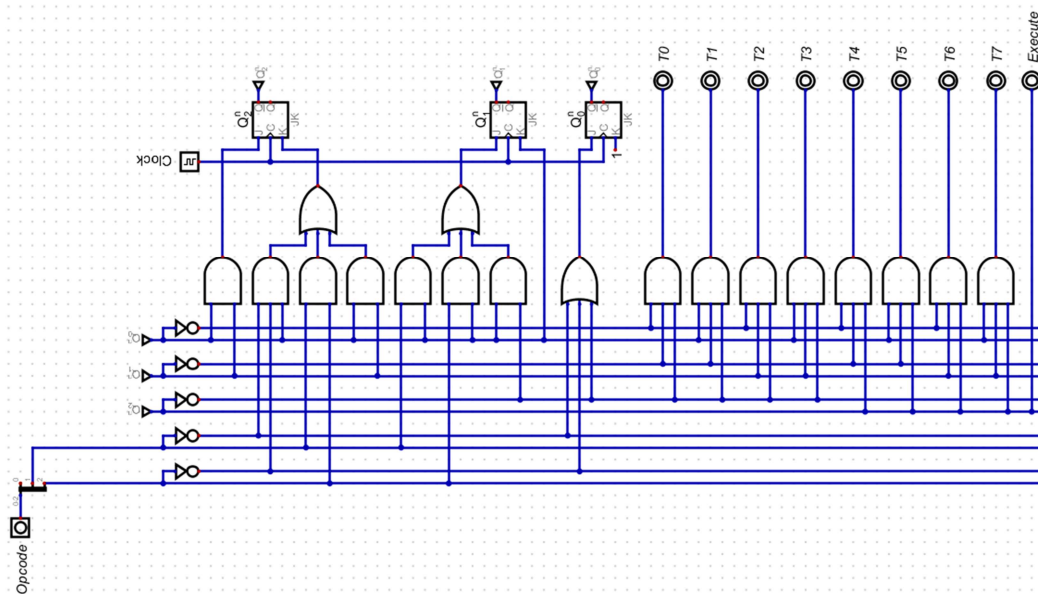

**Figure 4: Circuit for Instruction Sequencer FSM**

### 3 Numerical Verification

Shown in Figure 5, Figure 6, and Figure 7 are the numerical verification results, where an extensive set of input test vectors (Figure 5) were applied to the circuit.

Test data														
1	# Test vectors for control signals logic													
2	Clock Opcode T0 T1 T2 T3 T4 T5 T6 T7 Execute													
3	# Load instruction													
4	# MAR ← [PC]													
5	0	0	1	0	0	0	0	0	0	0	0	0	0	0
6	# IR ← [MAR]													
7	1	0	0	1	0	0	0	0	0	0	0	0	0	0
8	0	0	0	1	0	0	0	0	0	0	0	0	0	0
9	# ALU (Q) ← [PC]													
10	1	0	0	0	1	0	0	0	0	0	0	0	0	0
11	0	0	0	0	1	0	0	0	0	0	0	0	0	0
12	# PC ← [ALU]													
13	1	0	0	0	0	1	0	0	0	0	0	0	0	0
14	0	0	0	0	0	1	0	0	0	0	0	0	0	0
15	# MAR ← [IR]													
16	1	0	0	0	0	0	1	0	0	0	0	1	0	0
17	0	0	0	0	0	0	1	0	0	0	1	0	0	0
18	# DO ← [MAR]													
19	1	0	0	0	0	0	0	1	0	0	1	0	0	1
20	0	0	0	0	0	0	0	1	0	0	1	0	0	1
21	# Store instruction													
22	# MAR ← [PC]													
23	1	0	1	0	0	0	0	0	0	0	0	0	0	0
24	0	0	1	0	0	0	0	0	0	0	0	0	0	0
25	# IR ← [MAR]													
26	1	0	0	1	0	0	0	0	0	0	0	0	0	0
27	0	0	0	1	0	0	0	0	0	0	0	0	0	0
28	# ALU (Q) ← [PC]													
29	1	0	0	0	1	0	0	0	0	0	0	0	0	0
30	0	0	0	0	1	0	0	0	0	0	0	0	0	0
31	# PC ← [ALU]													
32	1	0	0	0	0	1	0	0	0	0	0	0	0	0

**Figure 5: Input Test Vectors**



Test result

File View

passed

	Clock	Opcode	T0	T1	T2	T3	T4	T5	T6	T7	Execute
L5	0	0	1	0	0	0	0	0	0	0	0
L7	1	0	0	1	0	0	0	0	0	0	0
L8	0	0	0	1	0	0	0	0	0	0	0
L10	1	0	0	0	1	0	0	0	0	0	0
L11	0	0	0	0	1	0	0	0	0	0	0
L13	1	0	0	0	0	1	0	0	0	0	0
L14	0	0	0	0	0	1	0	0	0	0	0
L16	1	0	0	0	0	0	1	0	0	0	1
L17	0	0	0	0	0	0	1	0	0	0	1
L19	1	0	0	0	0	0	0	1	0	0	1
L20	0	0	0	0	0	0	0	1	0	0	1
L23	1	0	1	0	0	0	0	0	0	0	0
L24	0	0	1	0	0	0	0	0	0	0	0
L26	1	0	0	1	0	0	0	0	0	0	0
L27	0	0	0	1	0	0	0	0	0	0	0
L29	1	0	0	0	1	0	0	0	0	0	0
L30	0	0	0	0	1	0	0	0	0	0	0
L32	1	0	0	0	0	1	0	0	0	0	0
L33	0	0	0	0	0	1	0	0	0	0	0
L35	1	1	0	0	0	0	1	0	0	0	1
L36	0	1	0	0	0	0	1	0	0	0	1
L38	1	1	0	0	0	0	0	1	0	0	1
L39	0	1	0	0	0	0	0	1	0	0	1
L42	1	0	1	0	0	0	0	0	0	0	0
L43	0	0	1	0	0	0	0	0	0	0	0
L45	1	0	0	1	0	0	0	0	0	0	0
L46	0	0	0	1	0	0	0	0	0	0	0
L48	1	0	0	0	1	0	0	0	0	0	0
L49	0	0	0	0	1	0	0	0	0	0	0
L51	1	0	0	0	0	1	0	0	0	0	0
L52	0	0	0	0	0	1	0	0	0	0	0
L54	1	2	0	0	0	0	1	0	0	0	1

Figure 6: Test Results (Table)

 


Figure 7: Test Results (Graph)

## 4 Summary

The problem requirement for this assignment was to design an Instruction Sequencer FSM circuit to generate the sequencing signals used to ensure the proper sequencing of the control signals generation for fetch and execute. To do so, the circuit must perform the dual function of generating the 8 timing pulses to sequence the fetch and execute operations as well as to generate the signal to indicate when the instruction is being fetched and executed.

The truth table and corresponding logical equations were essential to defining functionality and developing a logic expression, that was then used to specify a digital circuit solution. The digital circuit was tested with an extensive set of input vectors and produced the expected output for each test vector. Therefore, the specified digital circuit design solution satisfies the problem requirements.